

18-643 Lecture 7: Structural RTL Design

James C. Hoe

Department of ECE

Carnegie Mellon University

Housekeeping

- Your goal today: think about what you think about when you design “RTL”
- Notices
 - Handout #3: lab 1, **due noon, 9/22**
- Readings
 - HDL Compiler for Verilog Reference Manual and others at
</afs/ece/support/synopsys/2004.12/share/image/usr/local/synopsys/2004.12/doc/online/dc/print>
 - Vivado Design Suite User Guide: Synthesis (UG901)

Math


$$DFT_{n-m} = (DFT_n \otimes I_m) D_n^{n-m} (I_n \otimes DFT_m) L_n^{n-m}$$

Program/Algorithm



```

for (m = 0; m < mmax; m += 1) {
  for (i = m; i < n; i += istep) {
    j = i + mmax;
    tempr = wr*data[2*i] - wi*data[2*j+1];
    tempi = wr*data[2*j+1] + wi*data[2*i];
    data[2*i] = data[2*i] - tempr;
    data[2*j+1] = data[2*i+1] - tempi;
    data[2*i] += tempr; data[2*i+1] += tempi;
  }
}

```

 Schematic Capture

What do you see
in your mind when
you design hardware?

  *Dataflow**Hardware Description Language*


```

always @ (posedge Clk) begin
  if (a >= b) begin
    a <= a - b;
    b <= b;
  end else begin
    a <= b;
    b <= a;
  end
end


```

What is Structural Design?


Hardware Design is Structural

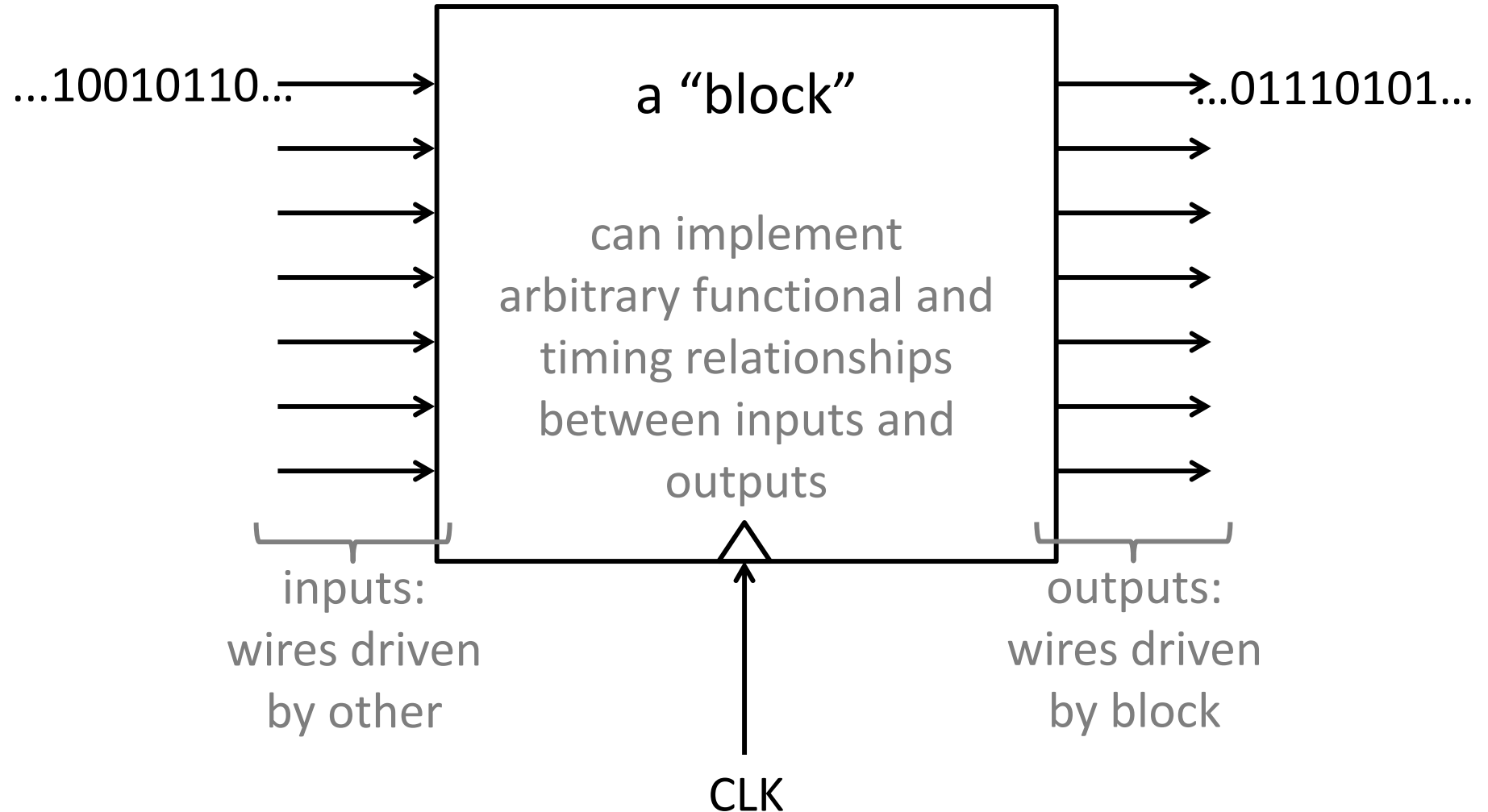

Hardware Design is Hierarchical

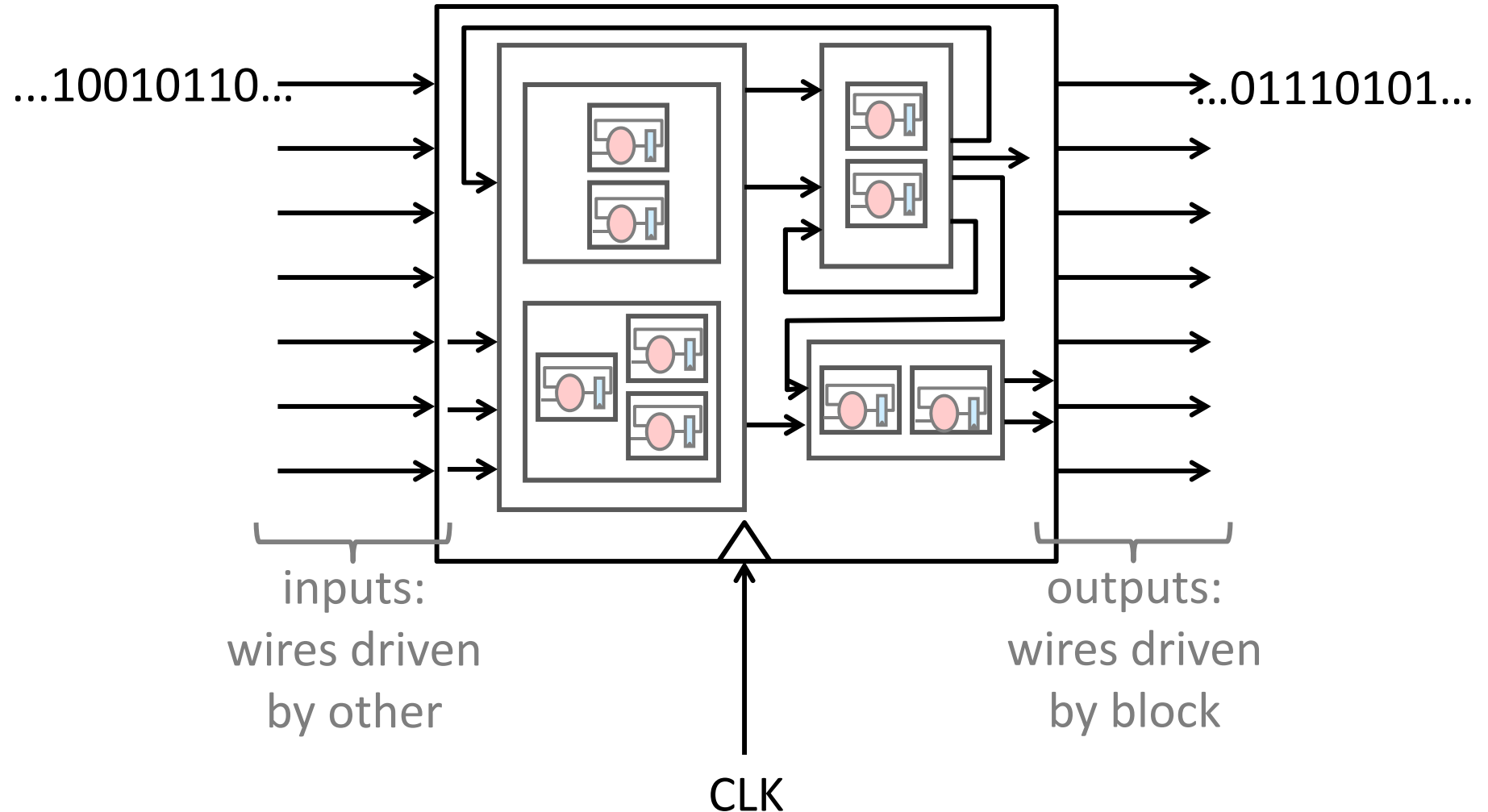


It all boils down to this

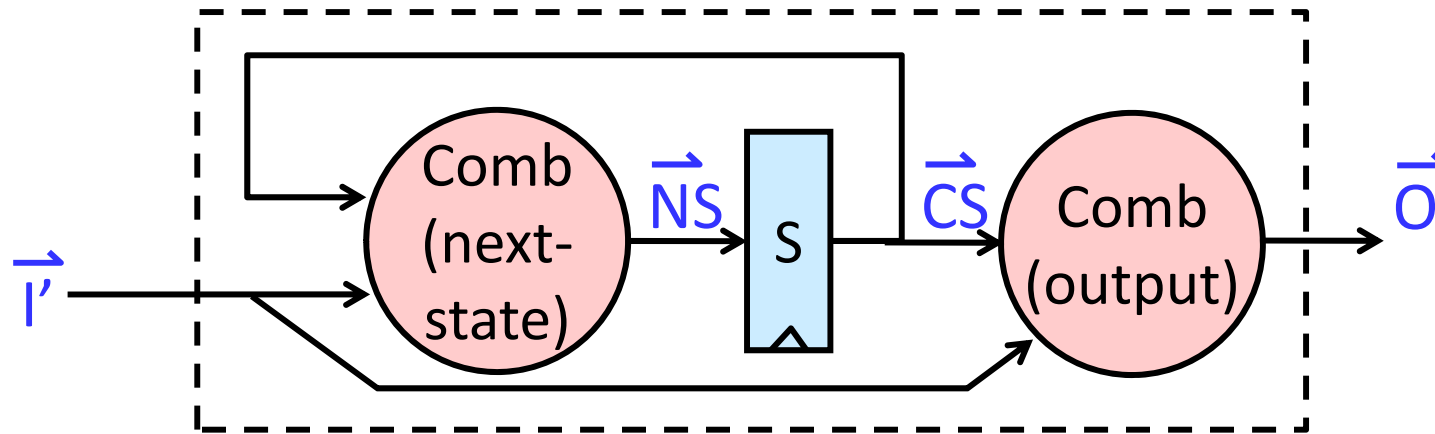




- a collection of **synchronous state** elements (updates on clock edge)
- a collection of **combinational** logic that computes next-state (\vec{NS}) from current-state (\vec{CS}) and input (\vec{I})
- a collection of **combinational** logic that computes output (\vec{O}) from current-state (\vec{CS}) and input (\vec{I})

Synchronous Timing

 

FSM-D

   
- datapath = “organized” combinational logic and registers to carry out computation (puppet)
- FSM = “stylized” combinational logic and registers for control and sequencing (puppeteer)





Cooperating FSM-Ds

 
- Partitioning large design into manageable chunks
 - natural decomposition by functionalities
 - inherent concurrency and replications
- Correct decomposition leads to simpler parts but coordination of the parts becomes the challenge
 - synchronization: having two FSM-Ds in the right state at the right time
 - communication: exchange information between FSM-D (requires synchronization)





Crux of the HW Design Difficulty

- We design FSM-Ds separately
 - liable to forget what one machine is doing when focusing on another
- No language support for coordination
 - no explicit way to say how state transitions of two FSMs must be related
- Coordination hardcoded into design implicitly
 - leave little room for automatic optimization
 - hard to localize design changes
 - (unless decoupled using request/reply-style handshakes)

 

“RTL” vs Schematics

- Same design abstraction
 - synchronous state, combinational next-state logic
 - hierarchy of modules with ports
- So why HDL more productive
 - textual description is easier, more compact
 - contemporary development in logic optimization (especially combinational)
 - procedural description of combinational logic
 - adopted PL know-hows: types, structs, operators, parameters, . . .
 - behavioral testbench

Better but not fundamentally different

Verilog an RTL language?

Verilog is not RTL

- Verilog in essence
 - a multithreaded programming language +
 - modeled time +
 - scheduling queue +
 - modules and ports
- Verilog describes how a module behaves, not its construction
 - no notion of “combinational” vs “sequential” logic
 - no notion of a register or even of a clock
 - perfectly happy describing non-hardware

Verilog Synthesis is Interpretation

```
// Ex 1
always@(a or b)
  if (a)
    c = b;
```

```
// Ex 2
always@(a)
  if (a)
    c = b;
  else
    c = 0;
```

```
// Ex 3
always@(a or b)
  if (a)
    c = b;
  else
    c = 0;
```

```
// Ex 4
always@(a or b)
begin
  c = 0;
  if (a)
    c = b;
end
```

```
// Ex 5
always@(a)
  if (a)
    c = b;
  else
    c = 0;

always@(b)
  if (a)
    c = b;
  else
    c = 0;
```

- All have well-defined behaviors
- According to Verilog semantics, **c** depends combinational on **a** and **b** in Ex 3, 4 and 5
- Verilog doesn't say they are "combinational" or they are synthesizable




Synthesizable Verilog

- Verilog becomes an RTL language and becomes synthesizable only when used in a stylized way dictated by the synthesis tool
- So called “synthesizable subset” is really a different language
- Difficult even to define what is “correct” synthesis with respect to simulation behavior

```
always@(a)  
  p = a & (!a);
```

= ?

 

Is **p** combinational?



RTL by Discipline


```
module contrived(input i, clk,
                 output o);
    reg cs; // sequential
    reg ns; // combinational
```

```
    assign o = cs;
```

```
    always @ ( i or cs )
        if (cs) ns = ~i;
        else   ns = i;
```

```
    always @ ( posedge clk ) begin
        cs <= ns;
    end
```

```
endmodule
```

 

} combinational


} synch. sequential



Crib sheet: Combinational “always”

- **f** must be assigned in all possible control paths; use “blocking” assigns
- **f** can depend on **f** only if **f** has been assigned
- repeated assigns to **f** okay; the last one holds
- **f** cannot be assigned in any other process
- multiple LHS vars okay; all rules above apply

“on all RHS vars”
always @* begin

 

end


Use continuous assigns for simple expressions



Crib sheet: Synchronous “always”


- use “non-blocking” assigns; effect of assign not visible until after all triggered processes are done
- f can depend on f ; RHS f stays at starting value
- repeated assigns to f okay; the last one holds
- f cannot be assigned in any other process
- multiple LHS vars okay; all rules above apply

always @(posedge clk) begin

 


end

Procedural Block to Combinational

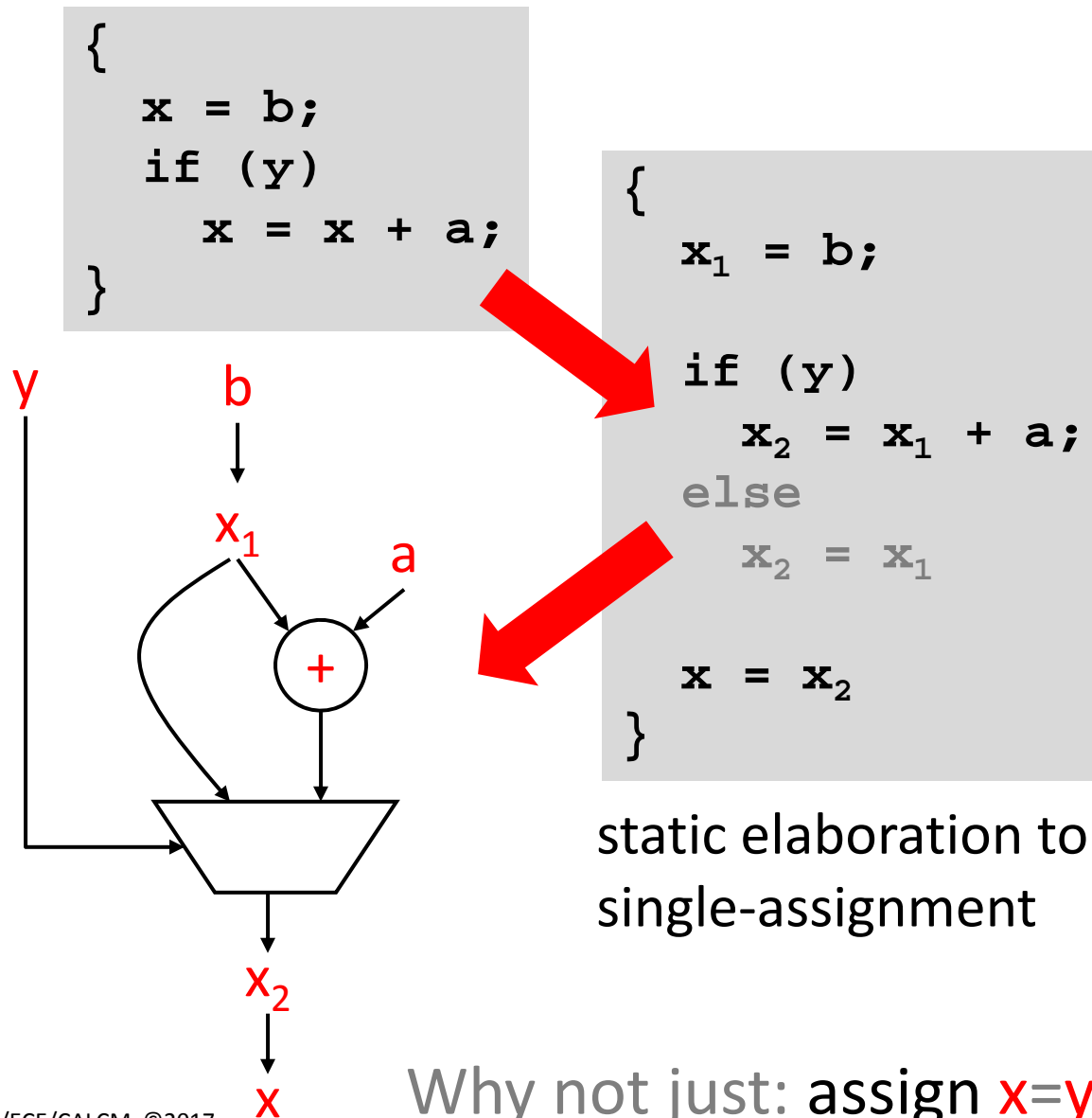

Why Procedural Block Wins
 
```
reg [5:0] Z;  
wire [31:0] A;  
  
integer i;  
  
always @(A) begin  
  
    Z=0;  
  
    for(i=0;i<=31;i=i+1) begin  
        if (A[i]) begin  
            Z=Z+1;  
        end  
    end  
  
end
```



Try saying this in continuous assign

Synthesizable Loops

- Loop must be statically unrolled, i.e.,
 - loop index must be integer type
 - loop index initial value must statically resolve to a constant
 - valid loop index operations are +, -
 - the valid loop condition test must test against a static limit using relational operators (<, <=, ==, etc)
- Precise limitations vary by tools and versions

Through static elaboration, even bounded-recursion should be okay

Don't try this at home

```
module fib( output [7:0] z, input [7:0] n );

    function [7:0] recur;
        input [7:0] n;
        begin
            if (n==0)
                recur=0;
            else if (n==1)
                recur=1;
            else
                recur=recur(n-1)+recur(n);
            end
        endfunction // recur

    assign z = recur(n);

endmodule
```

This is correct Verilog; does it synthesize?

Modern Synthesis Plays Tricks

- Standard compiler passes
 - constant propagation
 - common-subexpression elimination
 - deadcode elimination
 - strength reduction
- Bit-wise logic also Boolean optimized

Most of the time, good enough to write
understandable expressions with clear intent

Reserve Black Arts for Timing Closure

```
wire a, b, c, d;
wire [3:0] sel;
reg z;

always@* begin
    z = 0;
    if (sel[0]) z = a;
    if (sel[1]) z = b;
    if (sel[2]) z = c;
    if (sel[3]) z = d;
end
```




```
wire a, b, c, d;
wire [3:0] sel;
reg z;

always@* begin
    z = 0;
    if (sel[3])
        z = d;
    else if (sel[2])
        z = c;
    else if (sel[1])
        z = b;
    else if (sel[0])
        z = a;
end
```


Tool specific

Retiming

- Local transformations

 

 - Preserves I/O relationships
- Tools use retiming
 - balance critical paths
 - absorb FFs into hard macros



```
always@(posedge clk) begin
    a1<=a; b1<=b;
    a2<=a1; b2<=b1;
    c<=a2*b2;
end
```



Some Best Practices

- **#1** Read the style guides
- Develop a mental model of synthesis
- Know what optimizations tools do and don't do
- Know the special inference rules: FF, RAM, FSM
- Know pragmas to control the tool
- Read the synthesis reports (inference and warnings)

- Have a good naming convention
- Keep combinational and sequential distinct
- Use modules and hierarchies
- Embed assertions

FPGA Inference Extra Gotcha's

- FPGA Macros (especially RAM and DSP)
 - coarse functions and structures
 - some powerful but arbitrarily specific features
 - penalty is too huge to not get it right
- Very specific guideline for inferring hard macros
 - hard macros only does what it does
 - tools cannot recognize all “functional equivalent” descriptions

Always check inference report to see if
you got what you expected

Just on Flip-Flops

- Use asynch set or reset
 - ⇒ not all FFs have asynch reset; prevents DSP retiming
- Use both set and reset
 - ⇒ no FF has this; emulated externally with LUTs
- Use set and reset operationally
 - ⇒ set/reset cannot use special global lines
- Active-low set/reset and enables
 - ⇒ need LUTs to turn active-high

How could you know this?

- BRAM cannot be used if combinational read
- Shift registers can be made out of LUTs
 - BUT! no set/reset and can't read middle bits
- Registers will retime into multiplier and DSP (if no asynch reset)
- Use “initial” for power-on reset
- Timing analysis doesn't do “latches”
- Many, many more like this. . .

Read the inference report and warnings

RTMF!

Why is Structural Design Hard?



Reason #1: Low Level of Abstraction

- When writing a “high-level” program,
 - specify functionality using abstract constructs: loops, double, ‘+’, . . .
 - can ignore non-functional details: timing, data representation, data placement,
 - even assembly programming is in a virtualized realm
- When designing RTL
 - direct control of structure and operation
 - bit-level and cycle-level building blocks

**Say anything you want and get what you want;
but takes a whole lot more work**

Reason #2: Unrestricted Design Freedom



- Total freedom in how to realize a functionality

```
for(i=0; i<10; i=i+1)  
    sum+=i;
```

- is **sum** an integer or float, exactly how many bits?
 - how to ‘+’? ripple, c-select, c-look-ahead . . .
 - do ‘+’ one at a time or all at once?
 - where to store **i** and **sum**? may be not at all
- Can choose anything in between as “cheap as possible” (area or energy?) and as “fast as possible” (latency or throughput?)

Find the one right design in a haystack of bad ones



Reason #3: Massive Concurrency

- Extremely high degree of concurrency
- Extremely fine granularity of concurrency
- Explicit everything (synchronization, communication, . . .); poor language abstraction
- Nothing is disallowed (irregular parallelism, mixing parallelism, . . .)

Everything that makes parallel programming
hard is much worse in hardware design



Reason #4: Because it is hard

- Only design hardware as the last resort
 - if not performance critical, just write software
 - if not energy (or cost or weight) constrained, run on faster processors, bigger computers
 - if embarrassingly SIMD parallel, run on GPUs
- Unfortunately, what makes hardware design hard (#1~#3) is what makes hardware the ultimate weapon when all else fails

How to make hardware design easier
without making the results less efficient?

Parting Thoughts

- Know your tools and practice your craft
- Structural RTL design operates explicitly at the bit- and cycle-level
 - ➡ high workload requires large designs to be broken hierarchically into manageable modules
 - ➡ coordinating concurrent operations of distributed modules introduces its own “high” complexity
- Need better hardware design methodologies (without taking away hardware’s advantages)